

## Assess Quizzes from the o-book – Explanations for the answers.

## Chapter 8 Review – Support

Q	Reason
1	Ohmic means to have a constant relationship between V and I, thus it has to be linear and directly proportional. Hence, Graph A.
2	A fixed resistor means that its resistance doesn't vary no matter what voltage is applied or what current runs through it. In reality, it would be only guaranteed for a particular temperature such as 20°C or more commonly 70°C (maximum safe operating temperature).
3	Description of a metal and why it conducts. See page 209.
4	$V = IR$ $I = \frac{V}{R} = \frac{12}{100} = 0.12A$
5	$V = IR$ $R = \frac{V}{I} = \frac{8.0}{4.0 \times 10^{-3}} = 2000\Omega$
6	$V = IR$ $I = \frac{V}{R} = \frac{6}{3} = 2A$
7	$V = IR$ $I = \frac{V}{R} = \frac{12}{4} = 3A$ $3A = 3Cs^{-1}$ $Q = It = 3Cs^{-1} \times 1s = 3C$

## Assess Quizzes from the o-book – Explanations for the answers.

8	<p>Voltage (case 1) = voltage (case 2)</p> $V_1 = V_2$ $I_1 R_1 = I_2 R_2$ $\frac{I_1}{A_1} = \frac{I_2}{A_2} \text{ [as } R \propto \frac{1}{A}\text{]}$ $\frac{I_1}{\pi(r_1)^2} = \frac{I_2}{\pi(r_2)^2}$ $\frac{I_1}{\pi(r_1)^2} = \frac{I_2}{\pi(2r_1)^2} \text{ [diameter doubled means radius is doubled]}$ $\frac{I_1}{\pi(r_1)^2} = \frac{I_2}{4\pi(r_1)^2}$ $\frac{I_1}{\pi(r_1)^2} = \frac{I_2}{4\pi(r_1)^2}$ $I_1 = \frac{I_2}{4}$ $I_2 = 4I_1 = 4 \times 0.4$ $= 1.6 A$
9	$R_A = 6 \Omega,$ $R_B = 3 + 6 = 9 \Omega \text{ [series]}$ $\frac{1}{R_C} = \frac{1}{3} + \frac{1}{6} = \frac{2}{6} + \frac{1}{6} = \frac{3}{6} \quad A$ $R_C = \frac{6}{3} = 2 \Omega$ <p>Order is C, A, B [2, 6, 9 <math>\Omega</math>]</p>
10	<p>The resistance is just V/I for any point but it is linear so I could choose any pair of points. I have chosen 3 V, 0.6 A:</p> $V = IR$ $R = \frac{V}{I} = \frac{3.0}{0.60} = 5 \Omega$

## Assess Quizzes from the o-book – Explanations for the answers.

## Chapter 8 Review – Consolidate

Q	Reason
1	$L_2 = 2L_1$ $R_2 = 2R_1$ [as $R \propto L$ ] See page 230 $R_1 = \frac{V}{I_1} = \frac{12}{4} = 3\Omega$ $R_2 = 2R_1 = 2 \times 3 = 6\Omega$ $I_2 = \frac{V}{R_2} = \frac{12}{6} = 2A$
2	$V_1 = 3V$ (each branch is in series so $V_{\text{top}} = 1.5 + 1.5 = 3V$ ; $V_{\text{bottom}} = 1.5 + 1.5 = 3V$ . These two branches are in parallel so don't add, just use either. $V_1 = 3V$ . $V_2 = 1.5 + 1.5 + 1.5 + 1.5 = 6V$ (in series so add) $V_3 = 1.5 - 1.5 + 1.5 - 1.5 = 0V$ (in series but the direction of the 2 <sup>nd</sup> and 4 <sup>th</sup> cell is reversed so they are negative and cancel out) $V_4 =$ four in parallel and all the same so $V_4 = 1.5V$ Answer is 2.
3	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{6} + \frac{1}{2} = \frac{1+3}{6} = \frac{4}{6}$ $R_{eq} = \frac{6}{4} = 1.5\Omega$ $R_{total} = 1.5 + 6 = 7.5\Omega$ [in series]
4	Ohmic means a V/I graph (or I/V graph) is linear. If it is not linear it is non-ohmic.
5	At 0.55 V, the current is somewhere between 0.45 A and 0.5 A. Let's just say 0.5 A as it is not that clear. $R = \frac{V}{I} = \frac{0.55}{0.50}$

## Chapter 8 Review – Extend

Q	Reason
1	Looks about 35 mA when using the top scale (0-50 mA scale).

**Assess Quizzes from the o-book – Explanations for the answers.**

2	<p>Conventional current is from + (longer line on battery) around the external circuit to the negative (-) the smaller line on the battery. So current is anticlockwise.</p> <p>Meter M1 is in series with the circuit current so must be an ammeter. See page 214.</p> <p>Meter M2 is in parallel with the circuit current so must be a voltmeter. See page 220.</p>
3	<p><math>R \propto L</math> so will be linear graph (A).</p>
4	<p><math>R \propto \frac{1}{A}</math> so will be inverse (D)</p>
5	<p><math>R \propto L</math></p> <p><math>\frac{V}{I} \propto L</math></p> <p><math>\frac{1}{I} \propto L</math> [when V constant]</p> <p><math>I \propto \frac{1}{L}</math> [<math>y \propto \frac{1}{x}</math>]</p> <p>Inverse relationship so must be Graph D.</p>